CO200 - Computer Organization and Architecture


A2 - ALU and Register File Design in SystemC or Verilog


Points to Note

- Design and test each of the listed hardware modules in the SystemC or Verilog.
- In the comments section of the code, include a short description of the program, your name, roll number, date of writing the program and other information you deem relevant.
- (a) Report: Every question can have a corresponding answer containing block diagrams/ microarchitecture, brief explanation, other relevant info. (b) Auxiliary files to submit: Per question, include the following files along with the report: Code, the testbench including the monitor and stimulus, execution screenshots, VCD dump, gtkwave screenshots. (c) Archive: Organize your submission into directories per question.
- This is a team assignment. One submission per team.
- (a) Submission is due Oct. 31, midnight. Pack your report, code, screenshots and other files in an archive and mail to co200.nitk@gmail.com.

Modules

 - 1. **1-bit ALU**. Build a 1-bit ALU that can perform the following logical and arithmetic operations: AND, OR, NAND, NOR, ADD, SUBTRACT. Include two additional flags: (a) a flag to indicate if the result of the ALU operation is zero (Z), (b) a flag to indicate if the first input is greater than the second input. *Hint:* Reference implementation is described in Appendix B.5 in *Patterson and Hennesy, Computer Organization and Design, 5e, MK*.
- 2. **Register File**. Use the register designed above to implement a 32 register Register file with two read ports and one write port (Fig. shown below is the Figure B.8.7 from PH-COD-5e). The block diagrams of the two read ports and the write port are shown separately (Figures B.8.8 and B.8.9).



 

(a) Register File with two read ports.

(b) Write port implementation in the Register File.

Hint: For the block diagrams and design of the Register File refer Section B.8 of Patterson and Hennesy, Computer Organization and Design, 5e, MK.